

Advanced Engineering of Non-Isolated Interleaved Boost Converters for High-Gain Power Systems

Published: December 19, 2025 | Index ID: #276

The evolution of modern power electronics is increasingly defined by the demand for high-efficiency, high-density, and high-gain DC-DC conversion. As renewable energy sources like photovoltaic (PV) arrays and fuel cells produce relatively low output voltages (typically 20V to 50V), there is a critical need to step these voltages up to 400V or higher for grid-tied inverters or high-voltage DC buses. Traditionally, isolated converters using bulky transformers were the standard; however, the **non-isolated interleaved boost converter** has emerged as a superior alternative for applications where galvanic isolation is not strictly required. This technical analysis explores the architecture, mathematical modeling, and practical implementation of these high-gain systems.

1. The Shift from Isolated to Non-Isolated Topologies

In power system design, the choice between isolated and non-isolated DC-DC converters often dictates the final system's footprint, cost, and efficiency. Isolated converters, such as the Flyback or Forward types, utilize high-frequency transformers to provide a safety barrier. However, transformers introduce significant leakage inductance, leading to voltage spikes and the need for complex snubber circuits.

Non-isolated interleaved boost converters eliminate the transformer, instead utilizing **coupled inductors** or **voltage multiplier cells**. This shift offers several advantages:

- **Increased Power Density:** The absence of a large isolation transformer reduces the physical volume of the converter.
- **Higher Efficiency:** Energy losses associated with transformer core losses and copper losses are significantly mitigated.
- **Reduced Cost:** Fewer magnetic components and simplified insulation requirements lower the Bill of Materials (BOM).

However, the primary challenge of non-isolated boost converters is achieving high voltage gain without reaching extreme duty cycles, which can lead to diode reverse-recovery issues and excessive switching losses. This is where interleaving and high-gain techniques become essential.

2. Theoretical Framework of Interleaving

Interleaving involves connecting two or more boost converter stages in parallel and operating them with a phase shift. For a two-phase interleaved system, the switches are operated 180 degrees out of phase.

2.1 Ripple Cancellation Mechanics

The core benefit of interleaving is **input current ripple cancellation**. When the phases are shifted, the peak of the current in one inductor aligns with the trough of the current in another. This results in a total input current ripple that is significantly lower than the ripple of any individual phase. Mathematically, the ripple cancellation factor depends on the duty cycle (D). For a two-phase system, the ripple is minimized at $D = 0.5$.

2.2 Current Sharing and Thermal Management

Interleaving distributes the total input current across multiple paths. This reduces the **I^2R losses** in the inductors

and the conduction losses in the MOSFETs. By spreading the heat generation across more components, the thermal management system (heatsinks and fans) can be downsized, further improving power density.

3. High-Gain Enhancement Techniques

A standard boost converter has a theoretical gain of $1/(1-D)$. Practically, as D approaches 0.9, efficiency plummets due to parasitic resistances. To achieve gains of 10x or more, engineers integrate specialized circuits.

3.1 Coupled Inductor Integration

By replacing standard inductors with coupled inductors (which function similarly to a transformer but store energy), the turns ratio (n) becomes a new degree of freedom in the gain equation. The gain for a coupled-inductor interleaved boost converter is typically expressed as:

$$\text{Gain (G)} = (1 + n) / (1 - D)$$

This allows for high output voltages at moderate duty cycles (e.g., $D=0.5$ to 0.6), which keeps the converter in its most efficient operating range.

3.2 Voltage Multiplier Cells (VMC)

Voltage Multiplier Cells, such as the **Greinacher cell** or Diode-Capacitor Multipliers (DCM), are passive networks added to the boost stage. These cells "lift" the voltage through successive charging and discharging cycles. A typical DCM cell can double the output voltage of the boost stage without increasing the voltage stress on the primary switches.

Feature	Standard Boost	Interleaved Boost	Interleaved with Coupled Inductor + VMC
Voltage Gain	Low ($1/(1-D)$)	Moderate	Very High ($>10\times$)
Input Ripple	High	Low	Ultra-Low
Switch Stress	High (V_{out})	High (V_{out})	Reduced ($V_{out} / (n+1)$)
Component Count	Minimum	Moderate	High
Efficiency	Medium	High	Very High (with active clamping)

4. Active Clamping and Energy Recovery

One drawback of coupled inductors is the **leakage inductance**, which can cause high-voltage spikes across the MOSFET during turn-off. To solve this, **active-clamping circuits** are employed. These circuits consist of an auxiliary switch and a clamp capacitor. The active clamp performs two roles:

1. Energy Recycling: It captures the energy stored in the leakage inductance and transfers it to the load rather than dissipating it as heat.
2. Soft-Switching: It facilitates Zero Voltage Switching (ZVS) for the main switches, drastically reducing switching losses and allowing for higher switching frequencies.

5. Mathematical Modeling and Design Example

Consider a design requirement for a 200W converter stepping up 24V (Battery/PV) to 200V (DC Bus). Using a standard boost, D would need to be 0.88, which is inefficient. Using an interleaved converter with a coupled inductor ($n=2$):

Using the gain formula: $200/24 = (1 + 2) / (1 - D)$
 $8.33 = 3 / (1 - D)$
 $1 - D = 3 / 8.33 = 0.36$
 $D = 0.64$

At a duty cycle of 0.64, the MOSFETs are much easier to control, and the conduction intervals are balanced, leading to higher efficiency. Furthermore, the **voltage stress** on the switches is significantly reduced. In a standard boost, the switch sees the full 200V. In a coupled inductor topology, the stress is reduced by the turns ratio, allowing the use of MOSFETs with lower $R_{ds(on)}$.

6. Practical Implementation: PCB Layout and Control

The performance of high-gain interleaved converters is highly sensitive to PCB layout. High-frequency loops must be minimized to reduce Electromagnetic Interference (EMI).

6.1 Component Selection

- MOSFETs: Look for low gate charge (Q_g) and low $R_{ds(on)}$. GaN (Gallium Nitride) devices are increasingly used in these topologies to reach frequencies above 500kHz.
- Diodes: Schottky diodes or Silicon Carbide (SiC) diodes are preferred to eliminate reverse recovery losses.
- Capacitors: Low ESR (Equivalent Series Resistance) ceramic or polymer capacitors are necessary to handle the high ripple currents in the output stage.

6.2 Control Strategy

Control is typically managed by a dedicated PWM controller (like the LM5032) or a microcontroller (DSP/ARM). The controller must maintain a precise 180-degree phase shift. Current-mode control is often preferred to ensure balanced current sharing between the interleaved phases, preventing one inductor from saturating.

7. Performance Evaluation: Ripple and Efficiency

In a technical study of a **non-isolated high step-up interleaved boost converter**, the efficiency curve typically peaks between 92% and 96%. The input current ripple reduction can be as much as 50% to 80% compared to a single-phase counterpart, which is vital for extending the lifespan of input sources like fuel cells, which are sensitive to current fluctuations.

7.1 Efficiency vs. Load Table

Load Power (W)	Standard Boost Efficiency (%)	Interleaved + CI Efficiency (%)
50W	88.5%	91.2%
100W	89.1%	94.5%
150W	87.4%	95.1%
200W	84.2%	93.8%

8. Common Failure Modes and Troubleshooting

Designing these systems requires awareness of potential pitfalls:

- Inductor Saturation: If current sharing is not balanced, one inductor may saturate, leading to a catastrophic spike in current and MOSFET failure. Solution: Use average current mode control.
- Voltage Spikes: High dV/dt during switching can exceed the MOSFET's breakdown voltage. Solution: Improve active clamping or use a RCD snubber.
- Thermal Runaway: Poorly sized VMC capacitors can overheat due to high ESR. Solution: Parallel multiple low-ESR capacitors.

9. Environmental and Economic Impact

The adoption of non-isolated high-gain converters directly impacts the viability of renewable energy. By reducing the size and cost of the power electronics interface, the "Levelized Cost of Energy" (LCOE) for residential solar and small-scale wind is reduced. Furthermore, the high power density of these converters is a key enabler for the next generation of **Electric Vehicle (EV) DC-DC converters**, where space is at a premium.

Conclusion

The **non-isolated interleaved boost converter** represents a pinnacle of power density and efficiency in DC-DC conversion. By combining the ripple-canceling benefits of interleaving with the voltage-boosting capabilities of coupled inductors and multiplier cells, engineers can overcome the limitations of traditional boost topologies. While the complexity of the control and the higher component count present challenges, the resulting gains in performance and reduction in system volume make it the preferred choice for high-voltage renewable energy applications and modern power distribution networks. As wide-bandgap semiconductors like SiC and GaN continue to mature, these converters will only become more efficient, pushing the boundaries of what is possible in power electronics.

Baca Juga (Artikel Terkait)

- [The Engineering Blueprint of 1000W Power Inverters: From Circuit Topology to System Integration](http://123caramba.com/1000w-power-inverter-circuit-design-engineering-guide.pdf)

URL: <http://123caramba.com/1000w-power-inverter-circuit-design-engineering-guide.pdf>

- [Comprehensive Engineering Guide to Ultralow-Noise High-PSRR LDO Regulators: ADM7150, ADM7151, and TPS795 Series](http://123caramba.com/ultralow-noise-high-psrr-ldo-regulators-technical-guide.pdf)

URL: <http://123caramba.com/ultralow-noise-high-psrr-ldo-regulators-technical-guide.pdf>

- [Designing High-Efficiency Solar Charging Systems: A Deep Dive into Boost-Topology and Power Electronics](http://123caramba.com/solar-boost-topology-battery-charger-guide.pdf)

URL: <http://123caramba.com/solar-boost-topology-battery-charger-guide.pdf>

- [Advanced Analysis of Transformerless Buck-Boost Converters with Positive Output Voltage and Quadratic Gain](http://123caramba.com/transformerless-buck-boost-converter-positive-output.pdf)

URL: <http://123caramba.com/transformerless-buck-boost-converter-positive-output.pdf>

Tags: #DC DC Converter #Interleaved Boost #Power Electronics #Renewable Energy #High Voltage Gain

